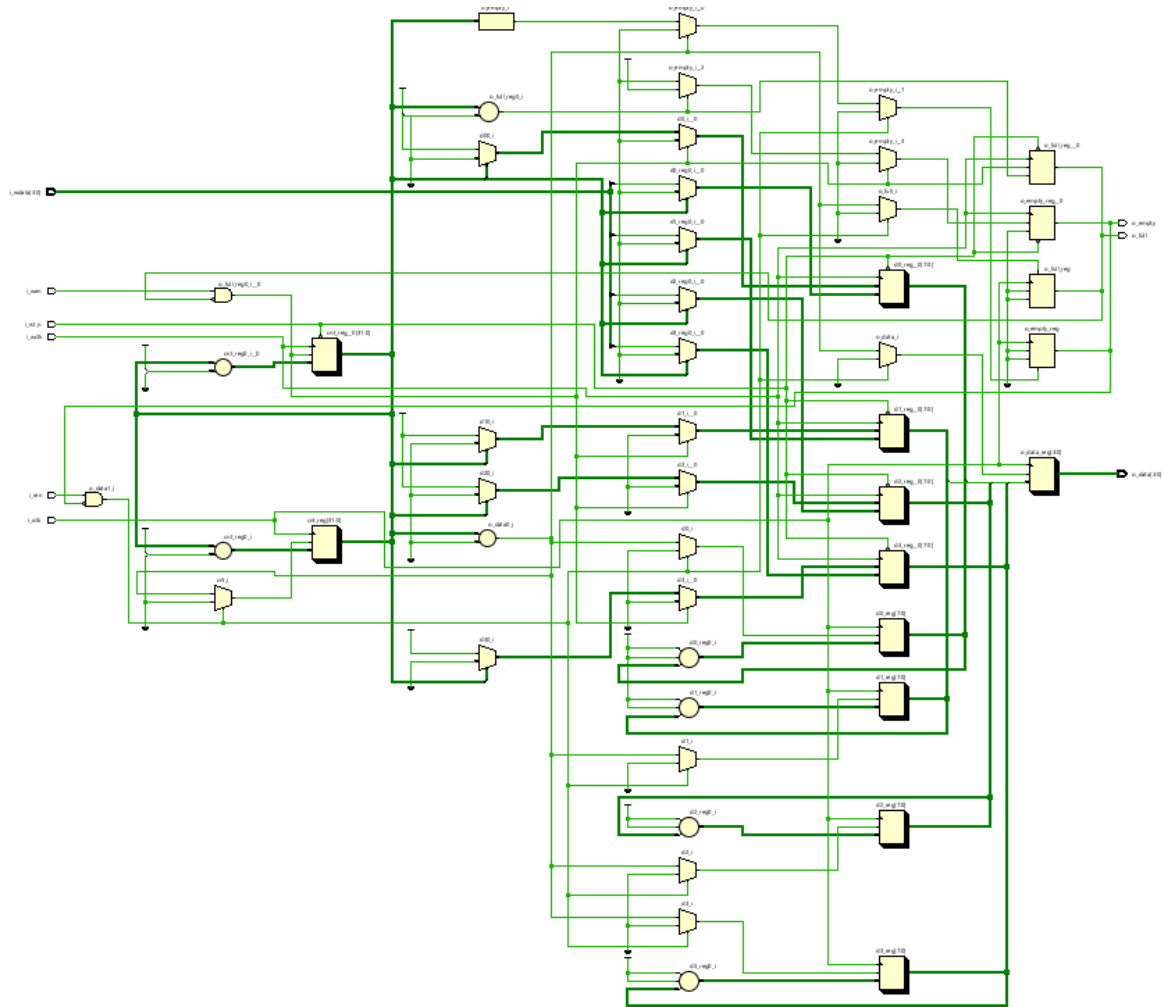


## Assignment 3

### Circuit Design:



Simulation waveform:

